

# Final Presentation

Design of a high-speed, multi-channel LVTTTL Level shifter board  
working with Swabian 8/2 Pulse Streamer and Acousto-optic modulators


# Content

1. Definition of Requirements
2. Prototyping Design
3. Manufacture and Assembly
4. Validation and Deployment
5. Conclusion



# Definition of Requirements

To improve from the previous design:

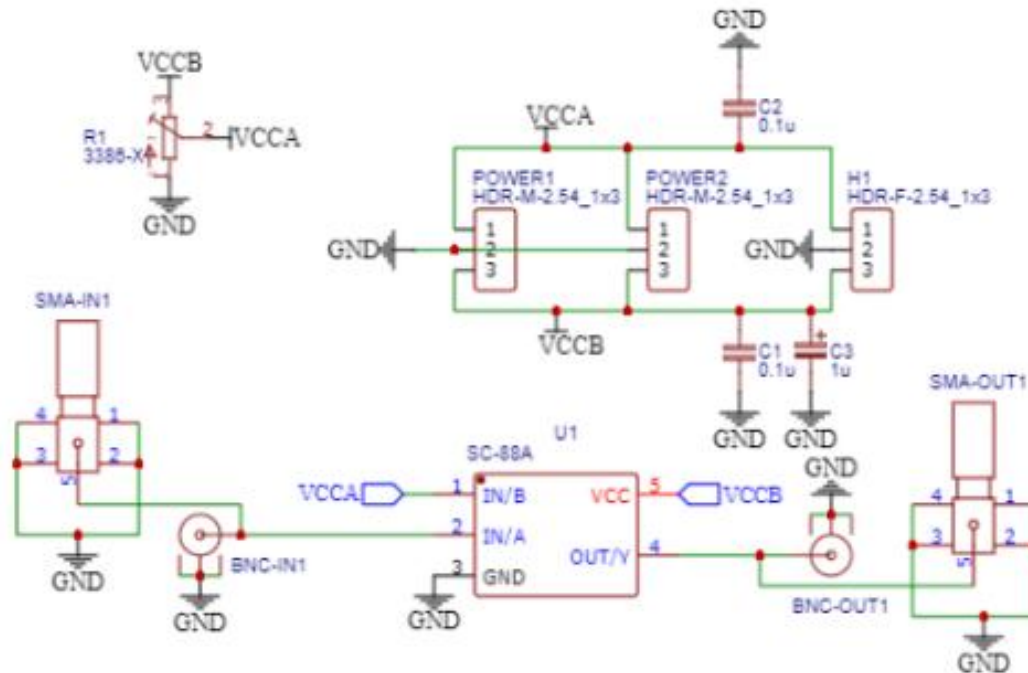


- Lack of circuit protection
- Needs manual tuning of potentiometer for translating different voltages
- Insufficient mechanisms to reduce crosstalks
- Single channel - messy power line connections for a typical setup


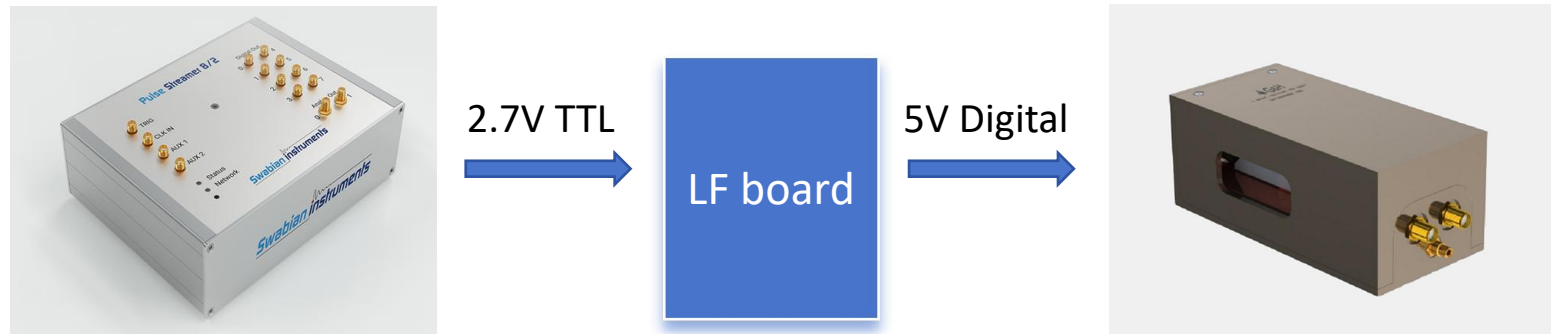
# Definition of Requirements


Hence, the design requirements:

- Level shifting with LVTTTL signals with rise/fall time 2-5ns and floating voltage levels from 2V to 3.3V
- Multi-channel board with common input and isolated outputs and a single power supply
- Circuit protection and cross-talk reduction


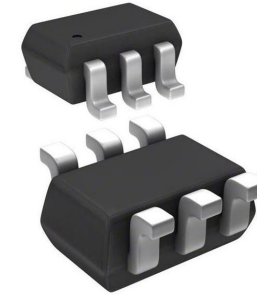
# Prototype Design - Components Selection

- NXU0101GM - 1 bit dual-supply translator with Schmitt-trigger
  - wide input range from 0.9V to 5V,
  - rise time & fall time ~ 1ns



- LP3982 - LDO Voltage Regulator with adjustable Vout
  - $R_1 = 162\text{k}\Omega, R_2 = 100\text{k}\Omega$   
→ Vout 3.3V

Use Equation 6 for adjusting the output to a particular voltage:

$$R_1 = R_2 \left[ \frac{V_o}{1.25\text{V}} - 1 \right]$$

Choose  $R_2 = 100\text{ k}\Omega$  to optimize accuracy, power supply rejection, noise, and power consumption.


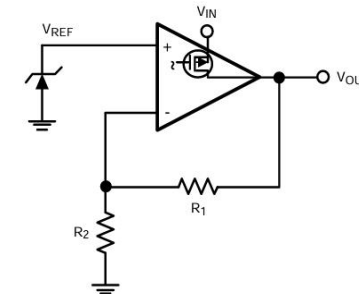


Figure 15. Regulator Topology Simplified

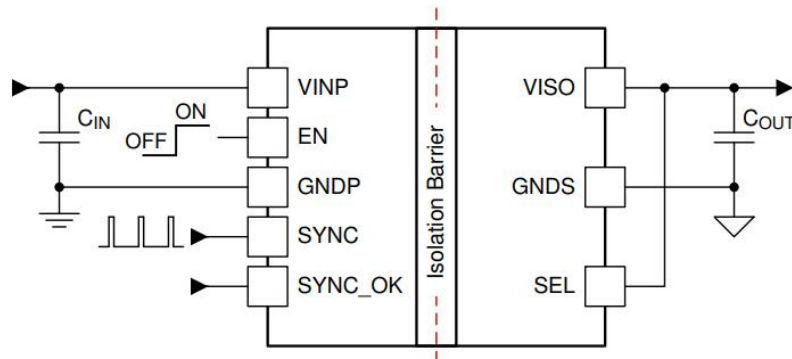


# Prototype Design - Components Selection


- For supplying isolated output signals to multiple AOMs,
  - UCC12051-Q1: High-efficiency Isolation DC/DC converter (Left)
  - ISO721M-EP: 5V High-speed digital Isolators (Right)
    - rise time & fall time  $\sim 1\text{ns}$ , max 150 Mbps signaling rate






Simplified Application

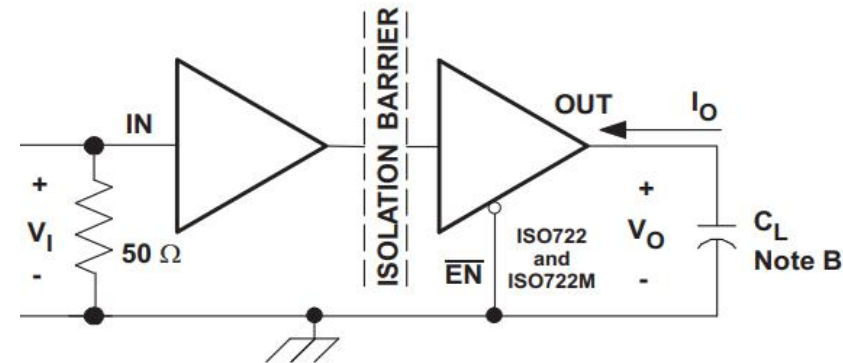

# Prototype Design - Block Diagram

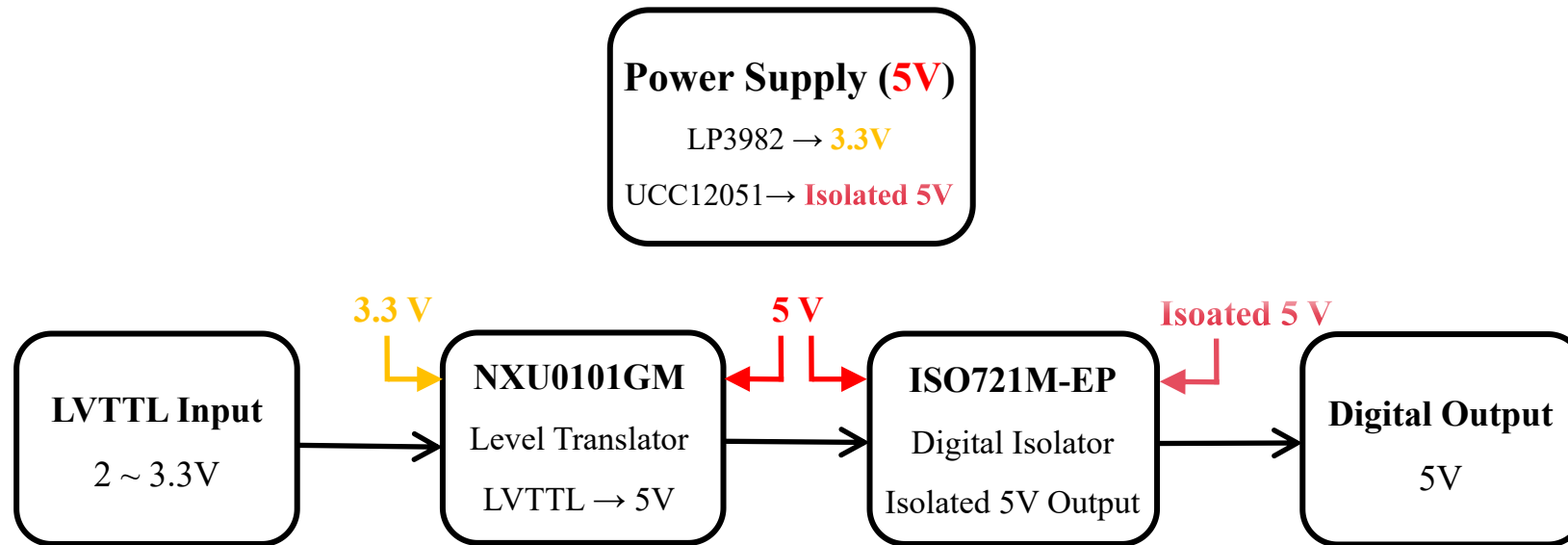


# Prototype Design - Schematics Design

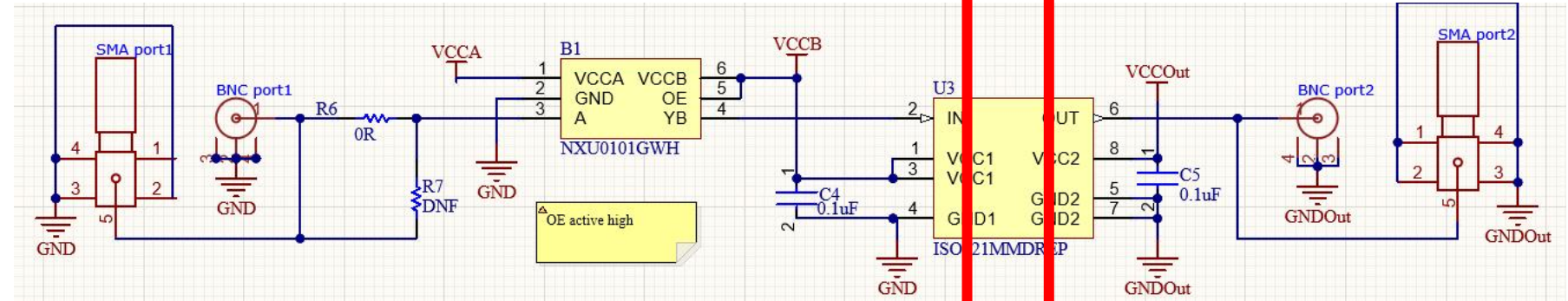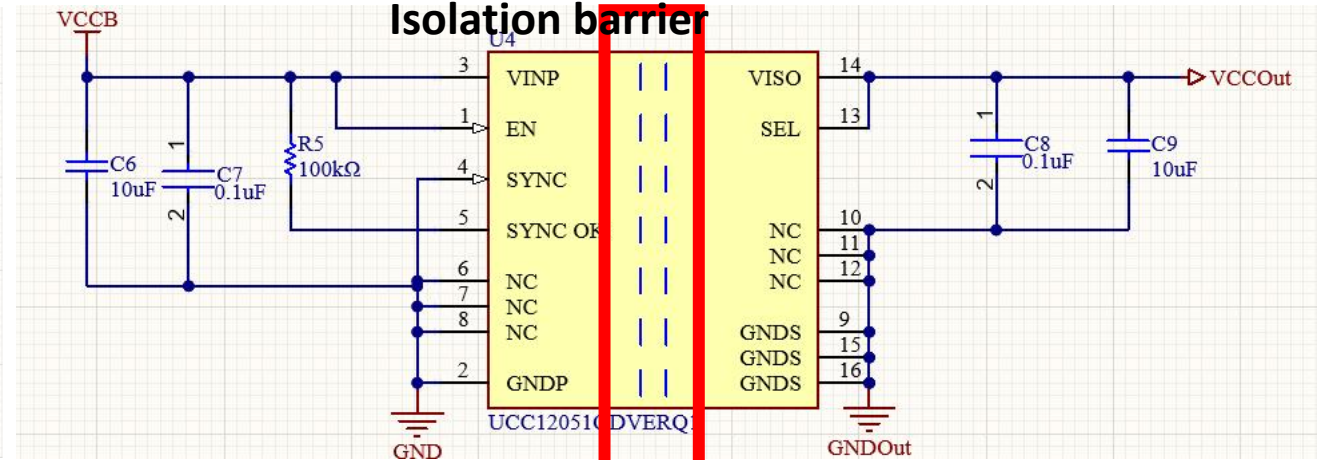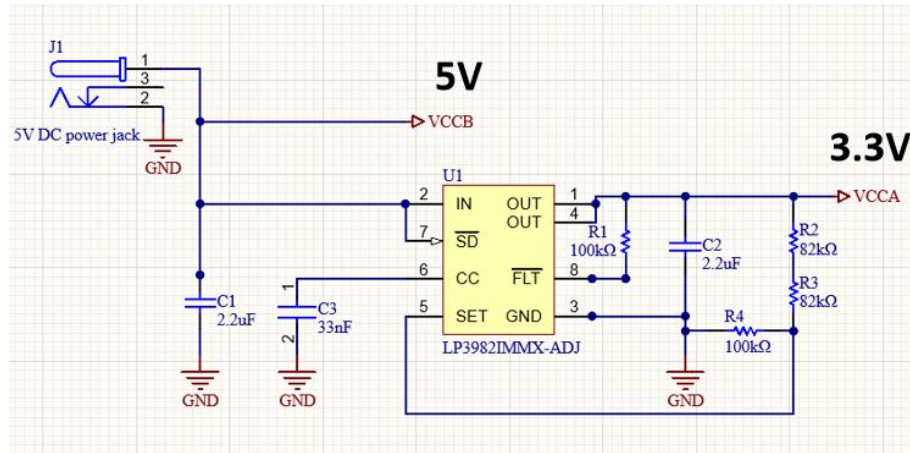



# Prototype Design - PCB Layout

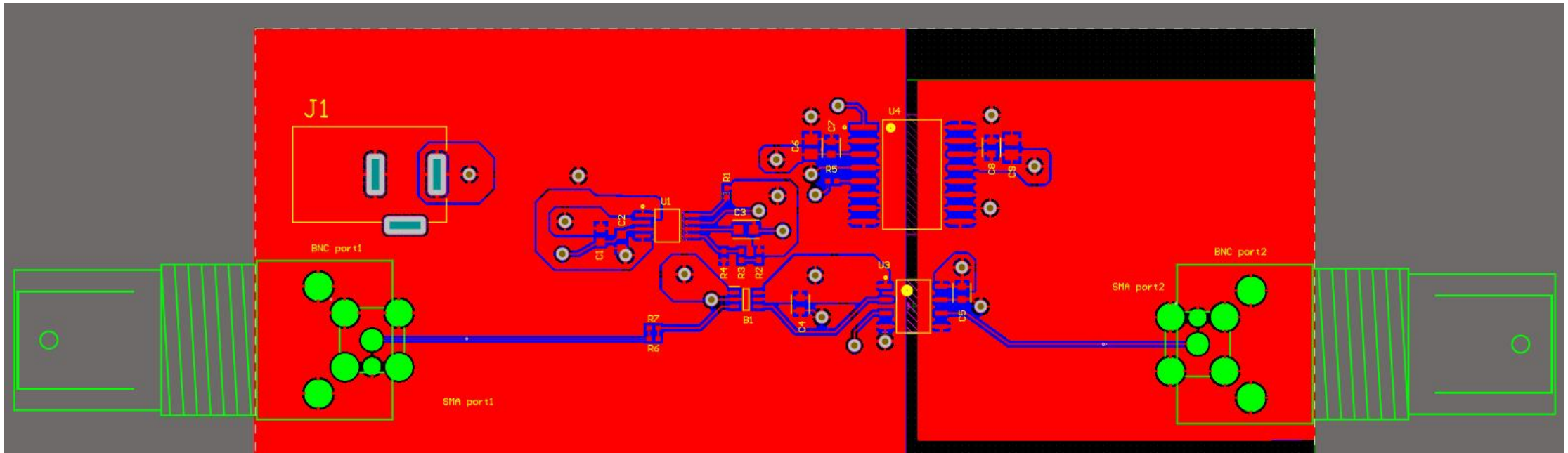

UNIVERSITY OF  
CAMBRIDGE

# Manufacture and Assembly - Cost

Part Number	Description	Manufacture	Supplier	Supplier Part Number	Unit Price	Quantity
NXU0101GWH	1 bit dual supply translator, Wide supply voltage range from 1.65 V to 5.5 V				\$0.22	4
CMP-2006-02273-1	2.2uF Ceramic capacitors	KEMET	Newark	07X0789	\$0.09	2
CMP-2006-04516-2	General Purpose Ceramic Capacitor, 0603, 33nF, 10%, X7R, 15%, 16V	Kyocera AVX	Arrow Electronics	0603YC333KAT2A	\$0.06	1

Pricing

Printed circuits



Basket nr.	Delivery term	PCB quantity	Unit price	Transport price	Transport mode	Total price	VAT	Gross
B4917171	3 Working days	5	22.14 GBP	8.08 GBP	Express	118.78 GBP	20.0 %	142.54 GBP

CMP-2002-07341-1	100kΩ resistor	Yageo	Newark	49AK1178	\$0.00	14
CMP-2002-05757-1	82k resistor	TE Connectivity	Farnell	2331569	\$0.01	2
CMP-0062-02330-3	LP3982, Micropower, Ultra Low-Dropout, Low-Noise, 300mA CMOS Regulator, 8-pin Mini SOIC	TI National Semiconductor			\$0.64	1
CMP-0328-00073-4	150 Mbps Enhanced Product Single Digital Isolator, 3.3 V / 5 V, -55 to +125 degC, 8-pin SOIC (D), Green (RoHS & no Sb/Br)	Texas Instruments	Arrow Electronics	ISO721MMDREP	\$7.86	4
CMP-04918-000737	AUTOMOTIVE, 500-MW, 5-KVRMS ISOL	Texas Instruments	Mouser	595-UCC12051QDVERQ1	\$4.62	4
Total					\$53.54	




UNIVERSITY OF  
CAMBRIDGE

# Manufacture and Assembly - Soldering

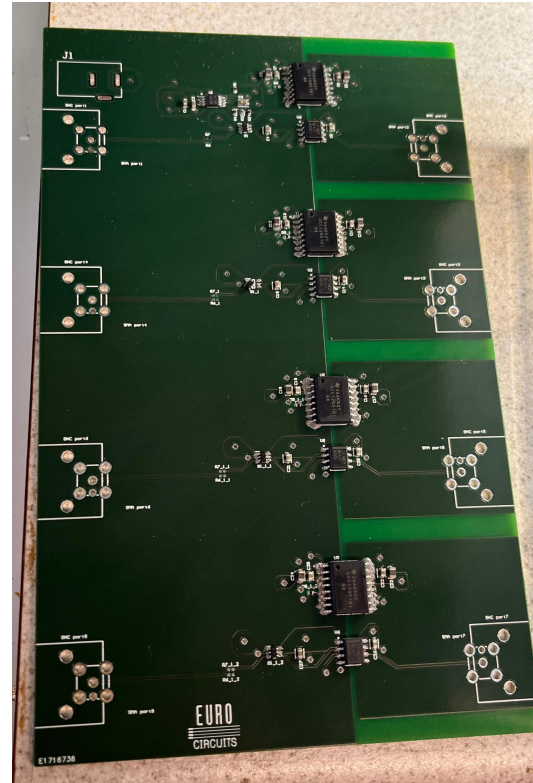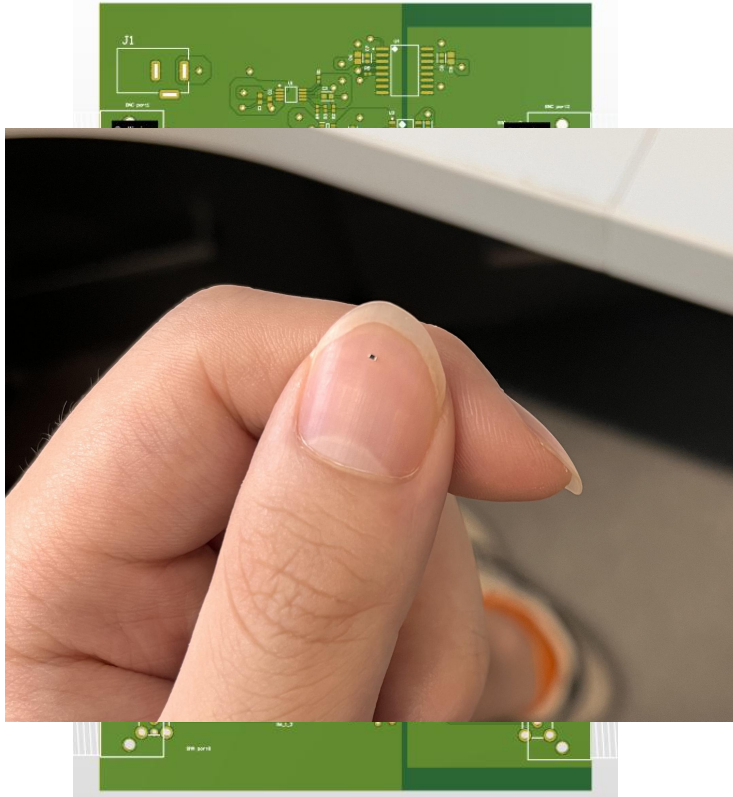

Surface-mount soldering

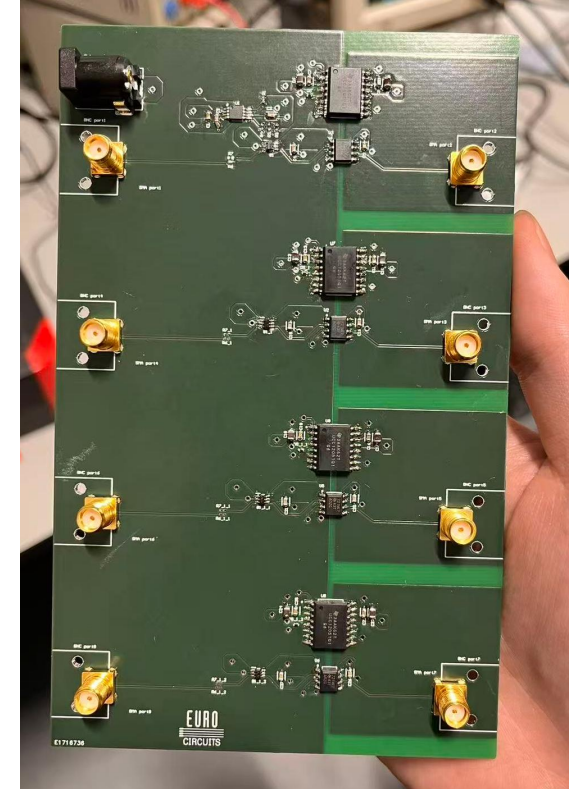


Through-hole soldering



UNIVERSITY OF  
CAMBRIDGE



# Validation and Deployment

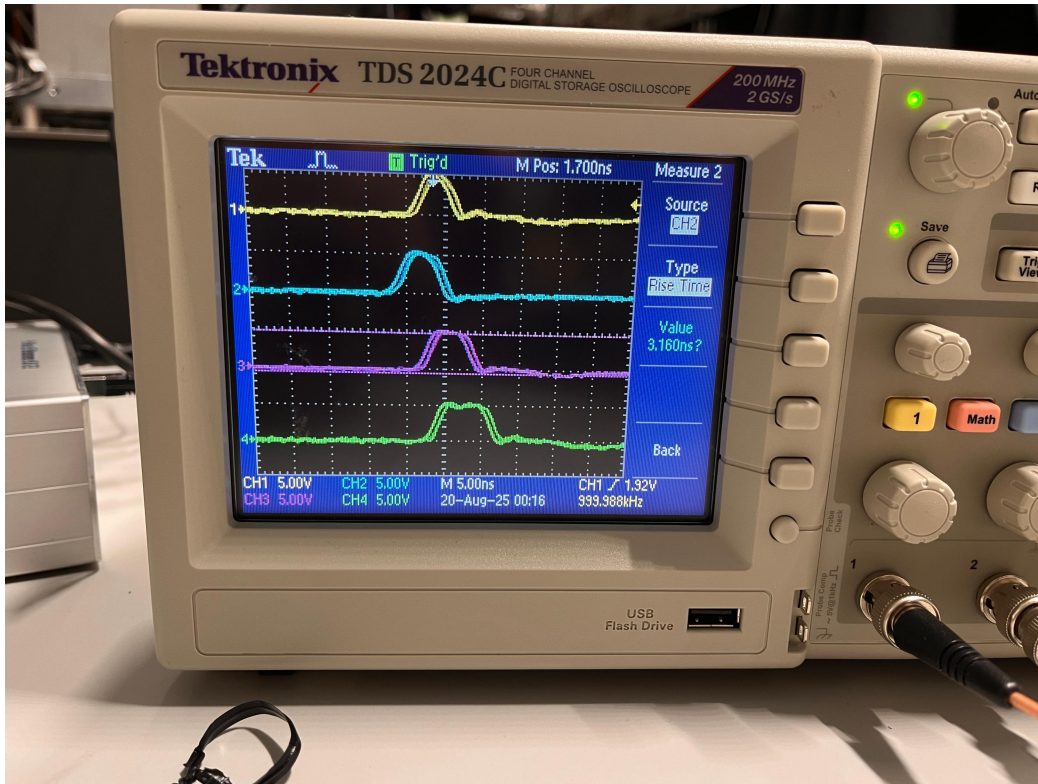

## Validation with Swabian 8/2 Pulse Streamer

- sending in 3ns, 4ns, 5ns and 7ns width pulse
- consistent 5V output with 2.7V TTL input
- approximately equal rise and fall time  $\sim 2\text{-}4\text{ ns}$
- no cross-talk between any output signals



UNIVERSITY OF  
CAMBRIDGE

# Validation and Deployment




**Four boards with SMA ports successfully deployed, the last one left for flexibility (BNC connection)**



**UNIVERSITY OF  
CAMBRIDGE**
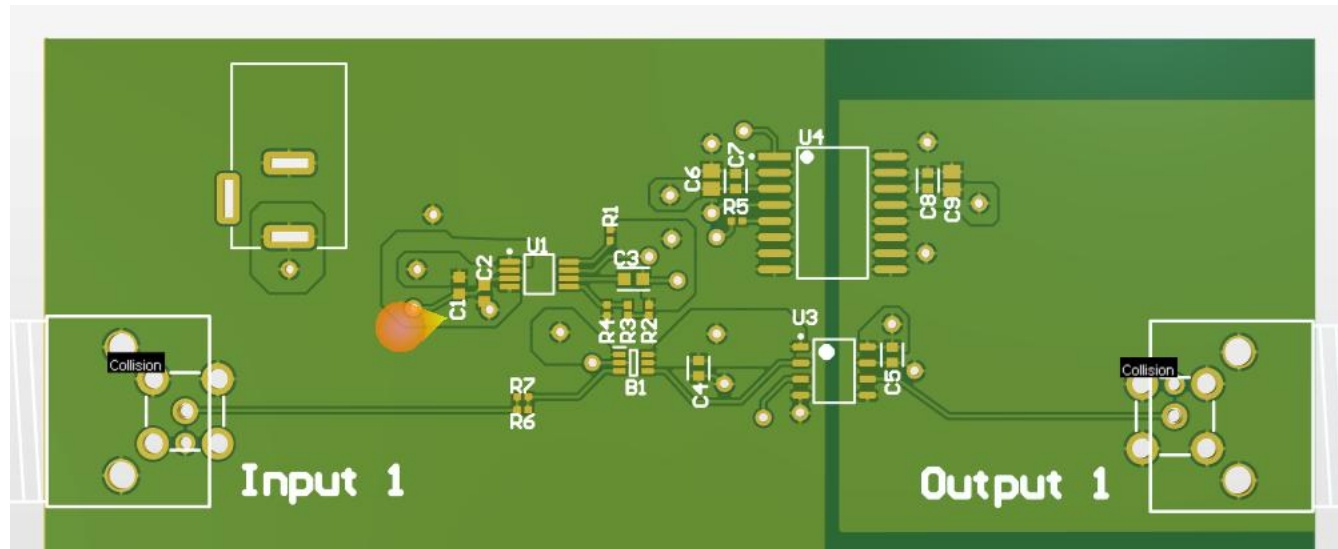
# Validation and Deployment - Further improvement



**Upload of the full project file to the teams electronics channel by the end of this week.**



**UNIVERSITY OF  
CAMBRIDGE**

# Conclusion

- Successfully designed and deployed 4 functional level shifter boards satisfying all the requirements defined:
  - protected, high-speed, 4-channel board with clean isolated outputs and a single power supply
- Learned about PCB design and manufacturing, surface-mount soldering, assembly and validation

